

# Electronic Devices and Circuits I - EE2CJ4

## Lab #2

-

2023 - 02 - 09

### Experiment - I

This is the case because of the entire premise of the Schmitt Trigger circuit. The Schmitt trigger seeks to convert a noisy-sinusoidal input into a smooth square wave. The two threshold voltages defined  $V_{th1}$  and  $V_{th2}$  are the voltages at which we transition from low to high. For example, if we are above  $V_{th1}$  we have a high output, and if we go below  $V_{th2}$  then we want a low output. For any region in between these (I.e.  $V_{th1} \leq V_{In} \leq V_{th2}$ ) then we want to stay in our current output state.

### Experiment - II

$(V_{ref}, R_1, R_2)$	$V_{th1}(theoretical)$	$V_{th2}(theoretical)$	$V_{gap}(theoretical)$
(0V, 4.7k $\Omega$ , 4.7k $\Omega$ )	2.5V	-2.5V	5V
<b>(0V, 22k<math>\Omega</math>, 4.7k<math>\Omega</math>)</b>	<b>0.88V</b>	<b>-0.88V</b>	<b>1.76V</b>
(2V, 4.7k $\Omega$ , 4.7k $\Omega$ )	3.5V	-1.5V	5V
(2V, 22k $\Omega$ , 4.7k $\Omega$ )	2.53V	0.77V	1.76V

- We are given the values of  $V_{ref}$ ,  $R_1$ ,  $R_2$ , and we are also told to assume that  $V_{sat+} = 5V$  and  $V_{sat-} = -5V$

- We know, from the background section of the lab manual, that...

$$V_{th1} = \frac{R_2}{R_2 + R_1} V_{sat+} + \frac{R_1}{R_2 + R_1} V_{Ref} \quad V_{th2} = \frac{R_2}{R_2 + R_1} V_{sat-} + \frac{R_1}{R_2 + R_1} V_{Ref} \quad V_{gap} = V_{th1} - V_{th2}$$

- Thus, performing a sample calculation on the bolded row above...

$$V_{th1} = \frac{4.7}{4.7 + 22} (5) + (0) = 0.88V$$

$$V_{th2} = \frac{4.7}{22 + 4.7} (-5) + (0) = -0.88V$$


$$V_{gap} = 0.88 - (-0.88) = 1.76V$$

### Experiment - III


$(V_{ref}, R_1, R_2)$	$V_{th1}(experimental)$	$V_{th2}(experimental)$	$V_{gap}(experimental)$
(0V, 4.7k $\Omega$ , 4.7k $\Omega$ )	2.7	-2.6	5.3
(0V, 22k $\Omega$ , 4.7k $\Omega$ )	0.9	-0.7	1.6
(2V, 4.7k $\Omega$ , 4.7k $\Omega$ )	3.6	-1.6	5.2
(2V, 22k $\Omega$ , 4.7k $\Omega$ )	2.385	0.64	1.745




(0V, 4.7kΩ, 4.7kΩ)

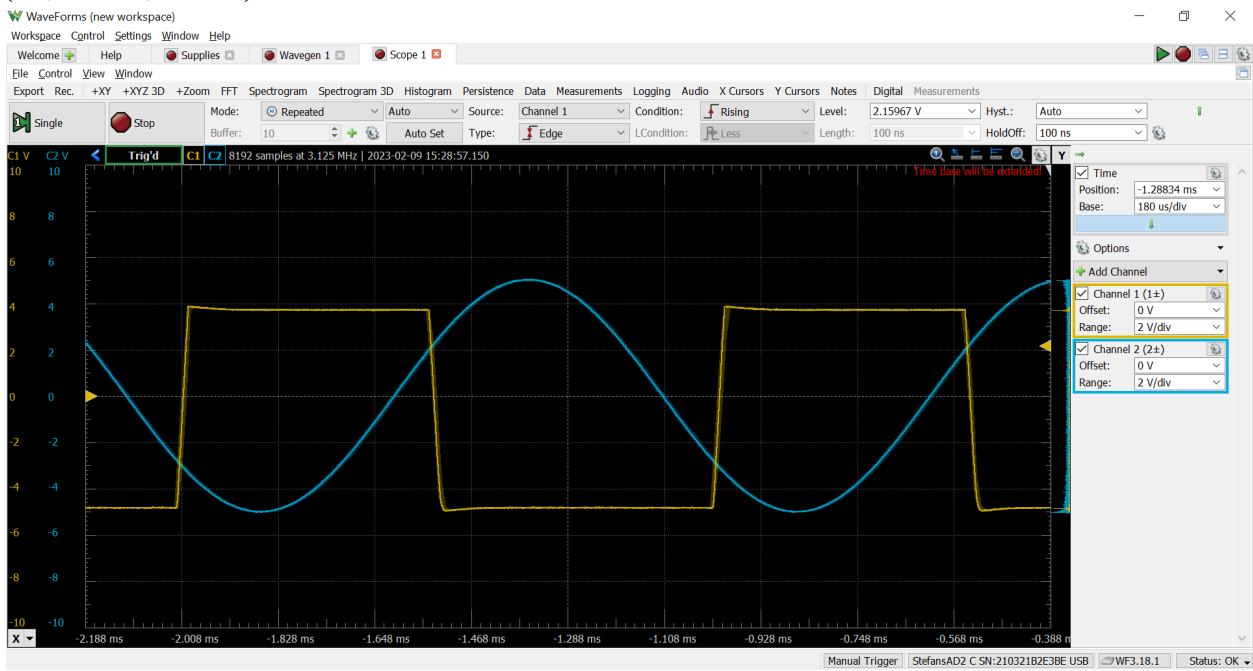


(0V, 22k $\Omega$ , 4.7k $\Omega$ )

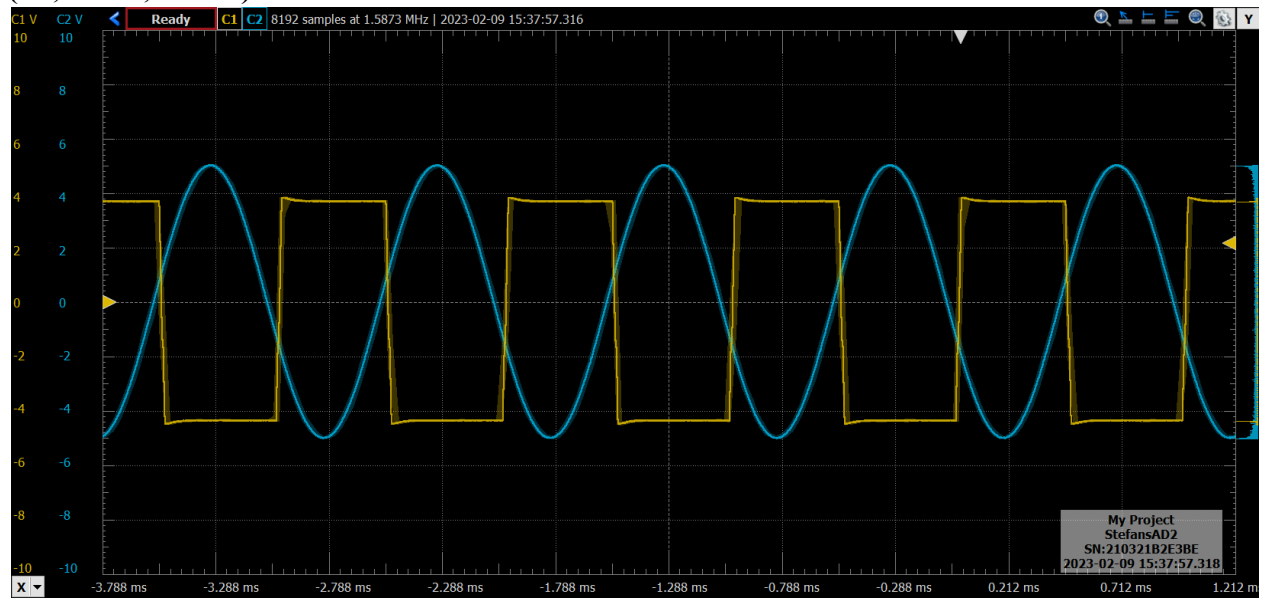

(2V, 4.7k $\Omega$ , 4.7k $\Omega$ )

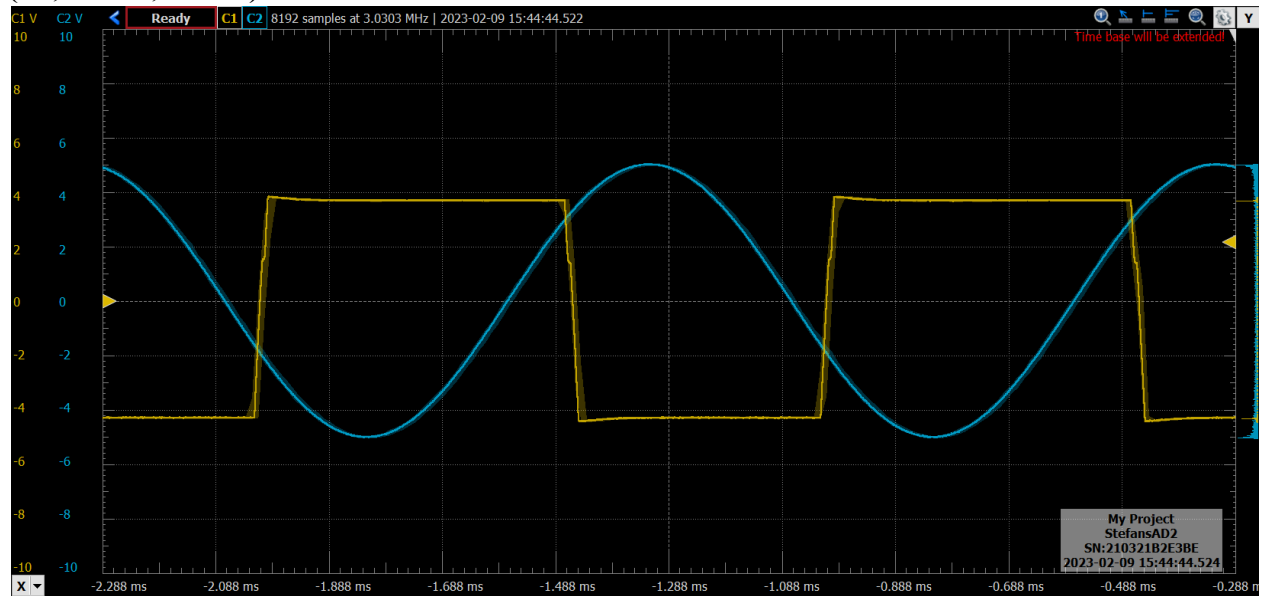

(2V, 22k $\Omega$ , 4.7k $\Omega$ )

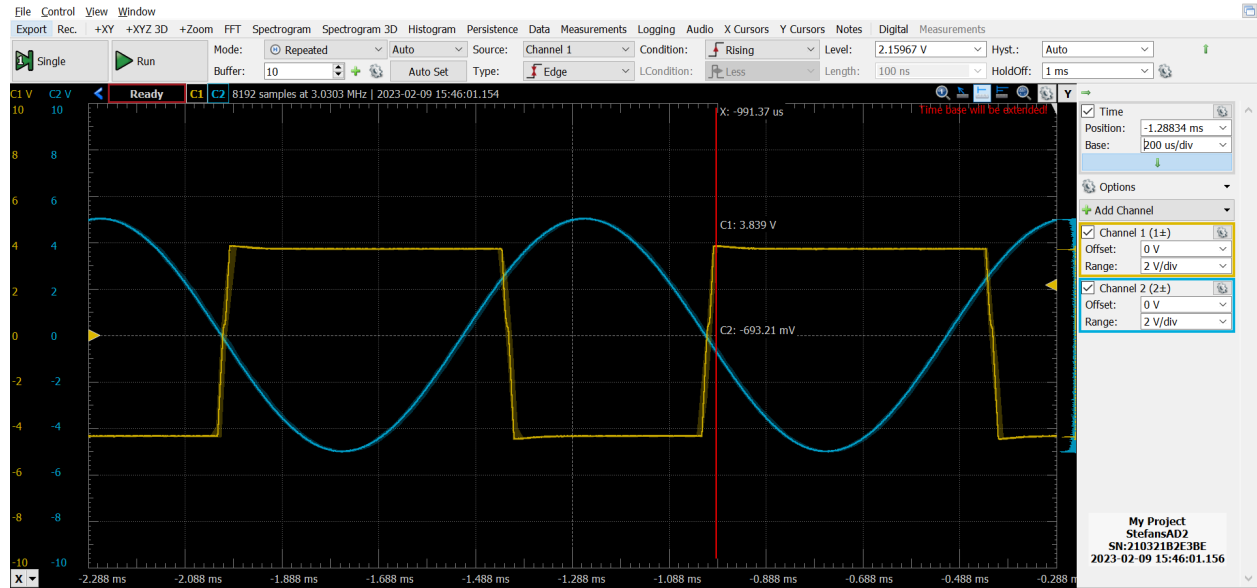

## Experiment - IV

$$\text{Error \%} = 100 - \frac{\text{Experimental} - \text{Theoretical}}{\text{Theoretical}} \times 100\%$$

$(V_{ref}, R_1, R_2)$	$V_{th1}(\text{Error \%})$	$V_{th2}(\text{Error \%})$	$V_{gap}(\text{Error \%})$
(0V, 4.7k $\Omega$ , 4.7k $\Omega$ )	7.4%	3.8%	5.6%
(0V, 22k $\Omega$ , 4.7k $\Omega$ )	2.3%	20%	9.1%
(2V, 4.7k $\Omega$ , 4.7k $\Omega$ )	2.86%	10%	4%
(2V, 22k $\Omega$ , 4.7k $\Omega$ )	5.7%	16.9%	0.9%

## Experiment - V

We noted that  $V_{gap}$  is not affected by  $V_{ref}$ . As we can see in our theoretical calculations, the reference voltage does not affect the gap voltage, the entire graph is shifted upwards or downwards by the value of the reference voltage, but the gap remains the same.